



Edited by Brad Thompson

Bandpass filter features adjustable Q and constant maximum gain

Herminio Martínez, Joan Domingo, Juan Gámiz, and Antoni Grau, Technical University of Catalonia, Barcelona, Spain

APPLICATIONS SUCH AS audio equalizers require bandpass filters with a constant maximum gain that's independent of the filter's quality factor, Q. However, all of the well-known filter architectures—Sallen-Key, multiple-feedback, state-variable, and Tow-Thomas—suffer from altered maximum gain when Q varies. **Equation 1** expresses the second-order bandpass transfer function of a bandpass filter:

$$H_{BP}(s) = K \frac{\left(\frac{s}{\omega_0}\right)}{\left(\frac{s}{\omega_0}\right)^2 + \frac{1}{Q}\left(\frac{s}{\omega_0}\right) + 1}, \quad (1)$$

where K represents the filter's gain constant. When the input frequency equals ω_0 , the filter's gain, A_{MAX} , is proportional to the product, KQ. Thus, modifying the quality factor alters the gain and vice versa.

This Design Idea describes a filter structure in which K is inversely proportional to Q. Altering Q also modifies K, producing a magnitude-plot set in which the curves maintain the same maximum gain at the central frequency ω_0 —that is, KQ remains constant. **Figure 1** shows the filter, which comprises a twin T cell with an adjustable quality factor and a differential stage. The differential stage comprises op amp IC₃ and resistors R_{5A} through R_{5D}. This stage outputs the difference between the filter's input signal and the twin-T network's output. Capacitors C₁ and C₂ are of equal value, C=C₁=C₂, capacitor C₃ equals 2C, resistors R₁ and R₂ are also equal and of value R=R₁=R₂, and R₃ equals R/2. **Equation 2** describes the twin-T circuit's transfer-function response as a notch filter producing output V_{BR}(t):

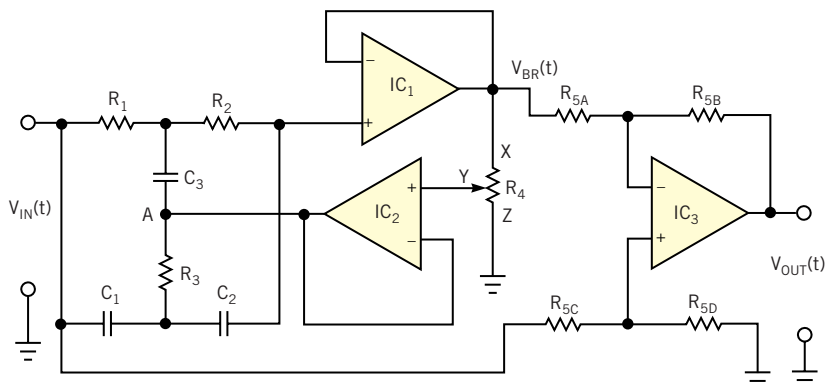


Figure 1 This bandpass active filter features adjustable Q and maximum gain in the passband and consists of a twin-T cell with Q adjustment and a differential output stage. You can also extract a frequency-notch output from the voltage-follower stage.

$$H_{BR}(s) = \frac{V_{BR}(s)}{V_{IN}(s)} = \frac{(RCs)^2 + 1}{(RCs)^2 + 4RC(1-m)s + 1}, \quad (2)$$

Equation 3 describes the complete circuit's transfer function, a bandpass-filter response with output V_{OUT}(t):

$$H_{BP}(s) = \frac{V_{OUT}(s)}{V_{IN}(s)} = \frac{4RC(1-m)s}{(RCs)^2 + 4RC(1-m)s + 1}, \quad (3)$$

where m represents the twin-T cell's feedback factor. If you designate R_{XY} as the resistance potentiometer R₄'s upper terminal, Point X; the rotor as Point Y; and R_{YZ} as the resistance between the rotor and the bottom terminal, Point Z, you can express m as the quotient of **Equation 4**:

$$m = \frac{R_{YZ}}{R_{XY} + R_{YZ}} = \frac{R_{YZ}}{R_4}. \quad (4)$$

Comparing **Equation 3** with the respective normalized transfer functions of a bandpass filter, **Equation 1**, **Equation 5** expresses the central frequency of the filter, ω_0 , coincident with the transmission zero of the twin-T network:

$$\omega_0 = \frac{1}{RC}. \quad (5)$$

Bandpass filter features adjustable Q and constant maximum gain.....71
 Moving-coil meter measures low-level currents72
 MOSFET enhances voltage regulator's overcurrent protection74
 Digitally programmable resistor serves as test load.....76

Publish your Design Idea in EDN. See the What's Up section at www.edn.com.

Equations 6 and 7, respectively, give quality factor Q and gain constant K:

$$Q = \frac{1}{4(1-m)}; \quad (6)$$

$$K = \frac{1}{Q} = 4(1-m). \quad (7)$$

The maximum gain, A_{MAX} , at $\omega = \omega_O$, always remains constant and equal to 1 (0 dB) and is independent of Q. The minimum quality factor is $1/4$ for $m=0$, which corresponds to the potentiometer's rotor connected to ground. The maximum gain is theoretically infinite, but, in practice, it's difficult to achieve a quality factor beyond 50. In most applications, Q ranges from 1 to 10.

Figure 2 shows the filter's magnitude and phase Bode plots for the frequency-notch output $V_{BR}(t)$ (available at IC₁'s output) for values of m from 0.1 to 0.9. Figure 3 shows Bode plots for the filter's bandpass output, $V_{OUT}(t)$, for the same values of m. In both graphs, frequency f_O equals 1061 Hz. To minimize frequency-response variations and improve response accuracy, you can build the filter with precision metal-film resistors of 1% or better tolerance. Likewise, use close-tolerance mica, polycarbonate, polyester, polystyrene, polypropylene, or Teflon capacitors. For best performance, avoid carbon resistors and electrolytic, tantalum, or ceramic capacitors. □

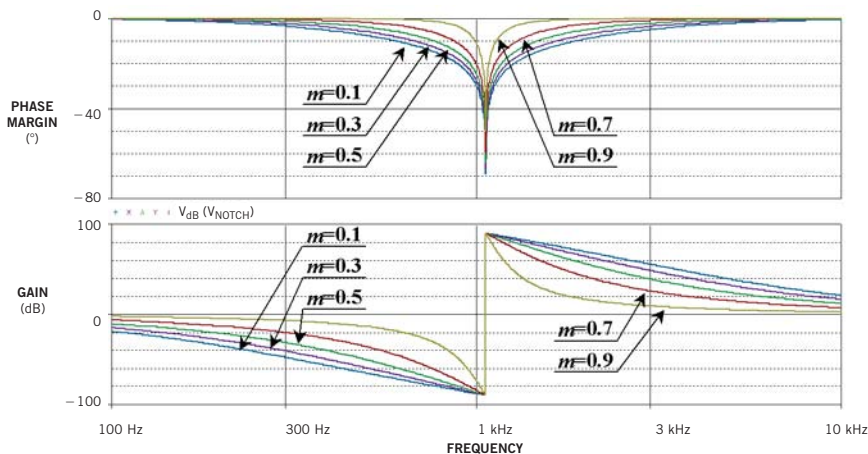


Figure 2

Magnitude and phase Bode plots at the frequency-notch output, $V_{BR}(t)$, show effects of varying twin-T-cell feedback factor, m, from 0.1 to 0.9.

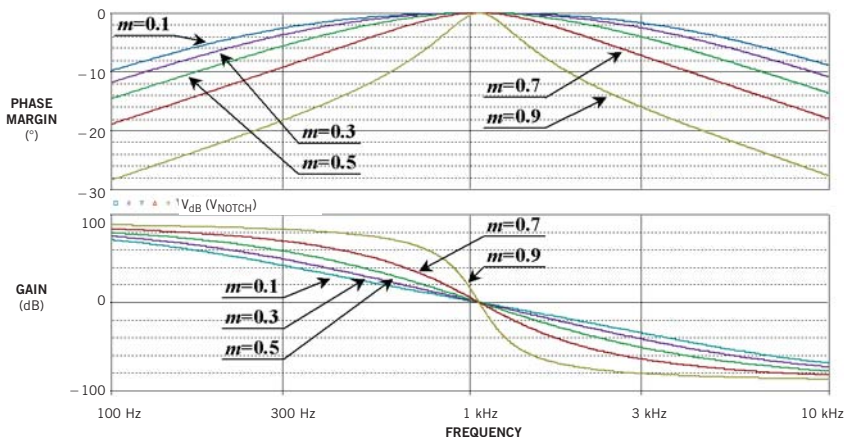


Figure 3

Magnitude and phase Bode plots at the bandpass output, $V_{OUT}(t)$, show effects of varying twin-T-cell feedback factor, m, from 0.1 to 0.9.